

1. PV Basics**Problems**

1.1. The ideal I-V characteristics of a solar cell, with cell voltage V_c and current I_c , can be written:

$$I_c(V_c) = I_{\text{photo}} - I_0 \cdot (e^{qV_c/nkT} - 1)$$

When parasitic resistance is present, the external voltage V and current I satisfy:

$$I(V) = I_c(V_c) - V_c/R_p = (V_c - V)/R_s$$

The parameters for various solar cells under various operating conditions are listed below:

(Assume $T = 300 \text{ K}$.)

<u>cell 1</u>	<u>cell 2</u>	<u>cell 3</u>	<u>cell 4</u>
$I_{\text{photo}} = 10 \text{ A}$	$I_{\text{photo}} = 15 \text{ A}$	$I_{\text{photo}} = 10 \text{ A}$	$I_{\text{photo}} = 10 \text{ A}$
$I_0 = 1.0 \times 10^{-16} \text{ A}$	$I_0 = 1.0 \times 10^{-16} \text{ A}$	$I_0 = 1.0 \times 10^{-14} \text{ A}$	$I_0 = 1.0 \times 10^{-16} \text{ A}$
$n = 1.0$	$n = 1.0$	$n = 1.0$	$n = 2.0$
$R_s = 0$	$R_s = 0$	$R_s = 0$	$R_s = 0.0 \Omega$
$R_p = 1.0 \times 10^8 \Omega$	$R_p = 1.0 \times 10^8 \Omega$	$R_p = 1.0 \times 10^8 \Omega$	$R_p = 1.0 \times 10^8 \Omega$

<u>cell 5</u>	<u>cell 6</u>	<u>cell 7</u>
$I_{\text{photo}} = 10 \text{ A}$	$I_{\text{photo}} = 10 \text{ A}$	$I_{\text{photo}} = 12.6 \text{ A}$
$I_0 = 1.0 \times 10^{-16} \text{ A}$	$I_0 = 1.0 \times 10^{-16} \text{ A}$	$I_0 = 4.0 \times 10^{-15} \text{ A}$
$n = 1.0$	$n = 1.0$	$n = 1.5$
$R_s = 0.1 \Omega$	$R_s = 0.0 \Omega$	$R_s = 0.05 \Omega$
$R_p = 1.0 \times 10^8 \Omega$	$R_p = 0.01 \Omega$	$R_p = 0.5 \Omega$

Determine the following device characteristics for each cell, including units:

- V_{OC} (open-circuit voltage)
 - I_{SC} (short-circuit current)
 - V_m (max.-power-point voltage)
 - I_m (max. power-point current)
 - P_m (max. power)
 - FF (fill factor)
-